

Ahsanullah University of Science and Technology
Department of Computer Science and Engineering

Course No : CSE 3110

Course Title : Digital System Design Lab

Assignment No : 02

Name of Experiment : 4×4 booth Multiplication

Date of Performance : 18 December, 2022

Date of Submission : 7th January, 2023

Submitted To : MD. Raqibul Hasan and Anika Rahman

Submitted By

Section : A

Lab Group : A2

Group No : 01

Group Members :

20200104029

20200104032

20200104037

20200104041

20200104046

Name of the Experiment: 4×4 booth multiplication

Problem Statement: Design a 4×4 multiplier.

Introduction: Booth's algorithm is a multiplication algorithm that can be multiply both positive and negative numbers. In this experiment, we made a

4×4 booth multiplier using "Booth's Algorithm".

It does not need a large number of additions or subtractions. It operates on the fact the

strings of 0's in the multiplier require just

shifting a string of the 1's in the multiplier

from bit weight 2^k to weight 2^m can be treated

as 2^{k+1} to 2^m .

Booth's Algorithm (Flowchart):


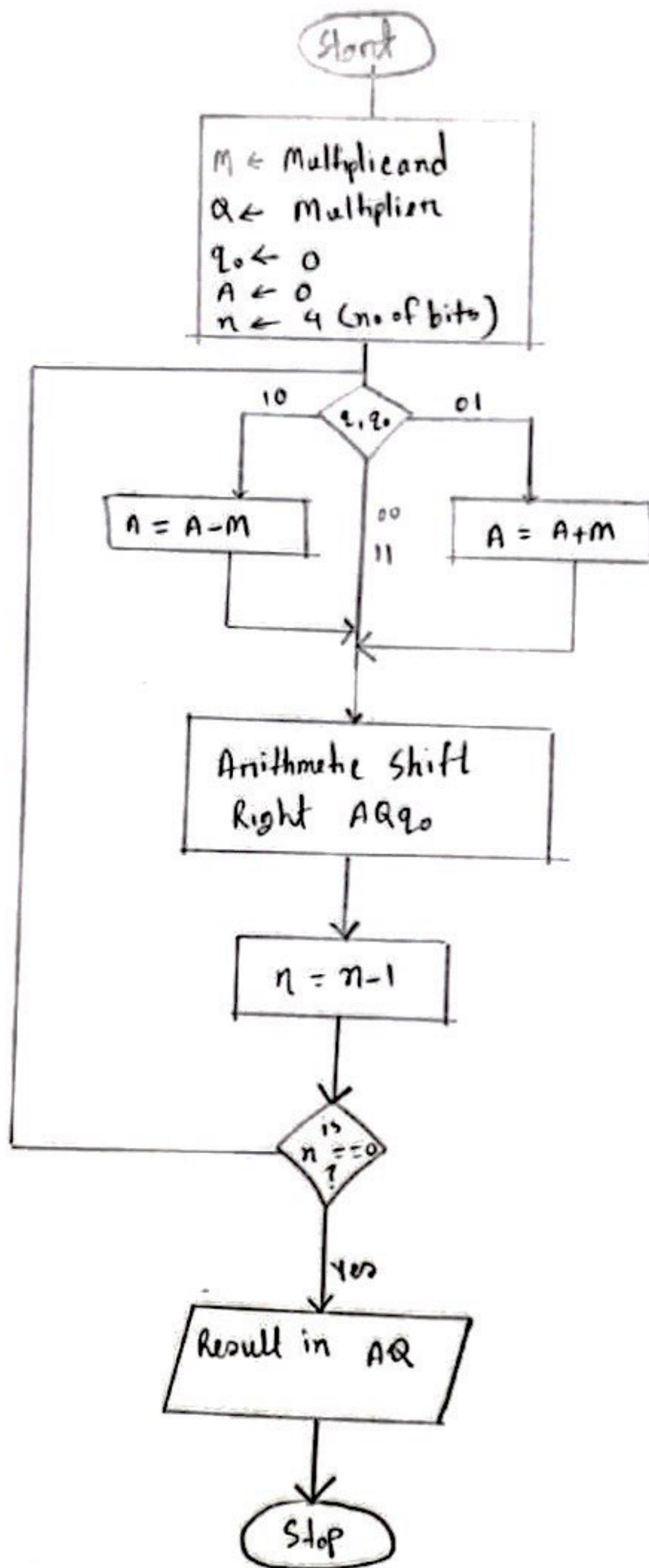


fig: Flowchart of Signed Multiplication
(Booth's Algorithm)


Circuit block diagram:

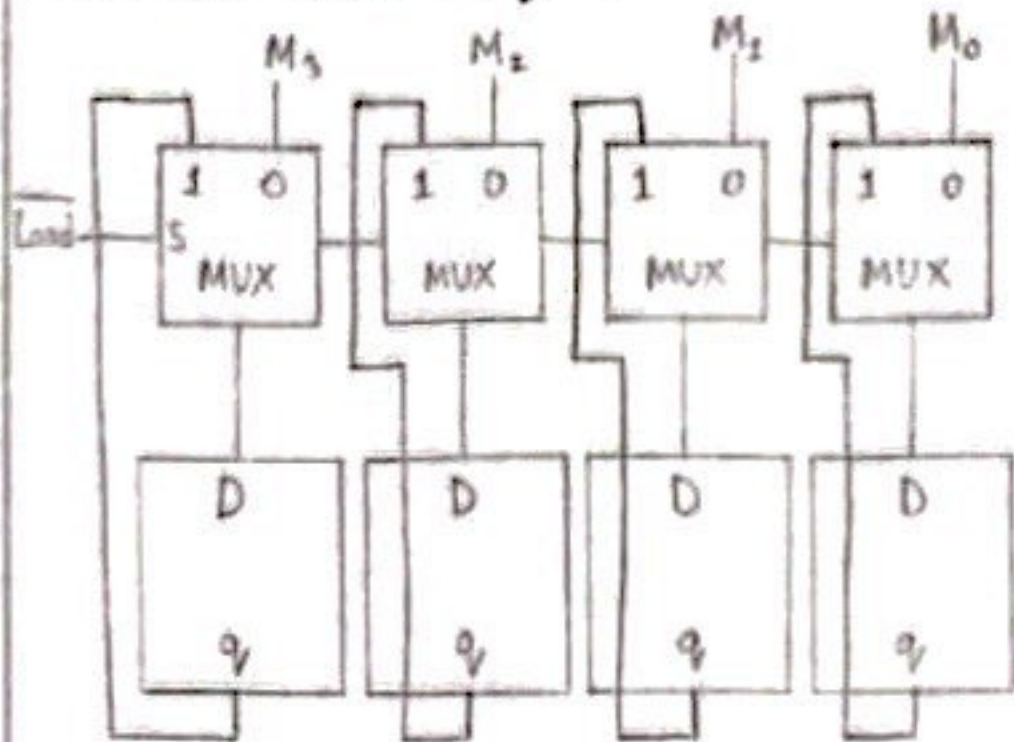

$Q_0 Q_{-1}$	Operator	X	Y	C_{in}
0 0	$A + 0$	A	0	0
0 1	$A + M$	A	M	0
1 0	$A - M$	A	\bar{M}	1
1 1	$A + 0$	A	0	0


$$Y = \overline{Q_0} Q_{-1} M + Q_0 \overline{Q_{-1}} \overline{M}$$

$$C_{in} = Q_0 \overline{Q_{-1}}$$

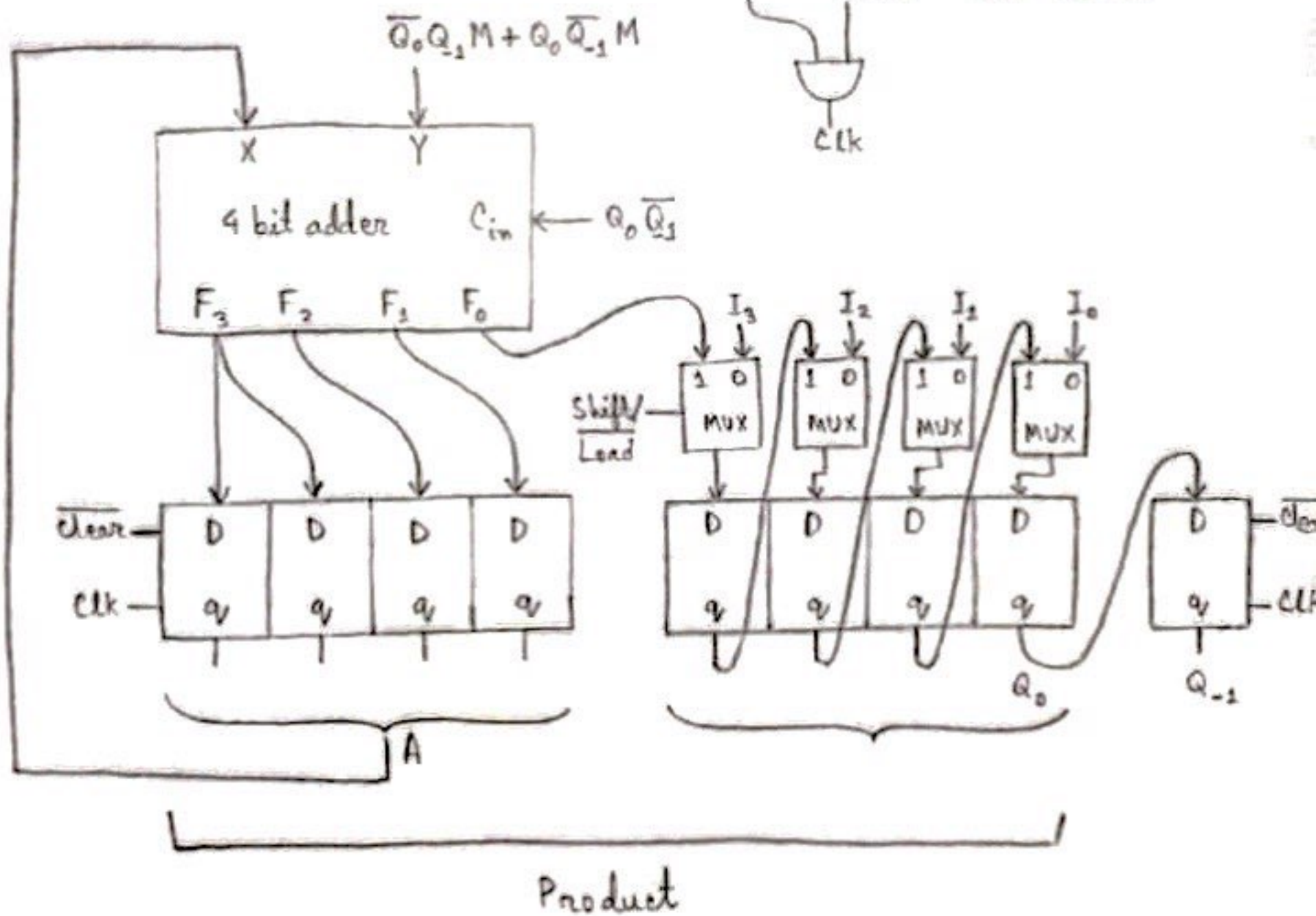

Control Unit Design:

State Diagram:

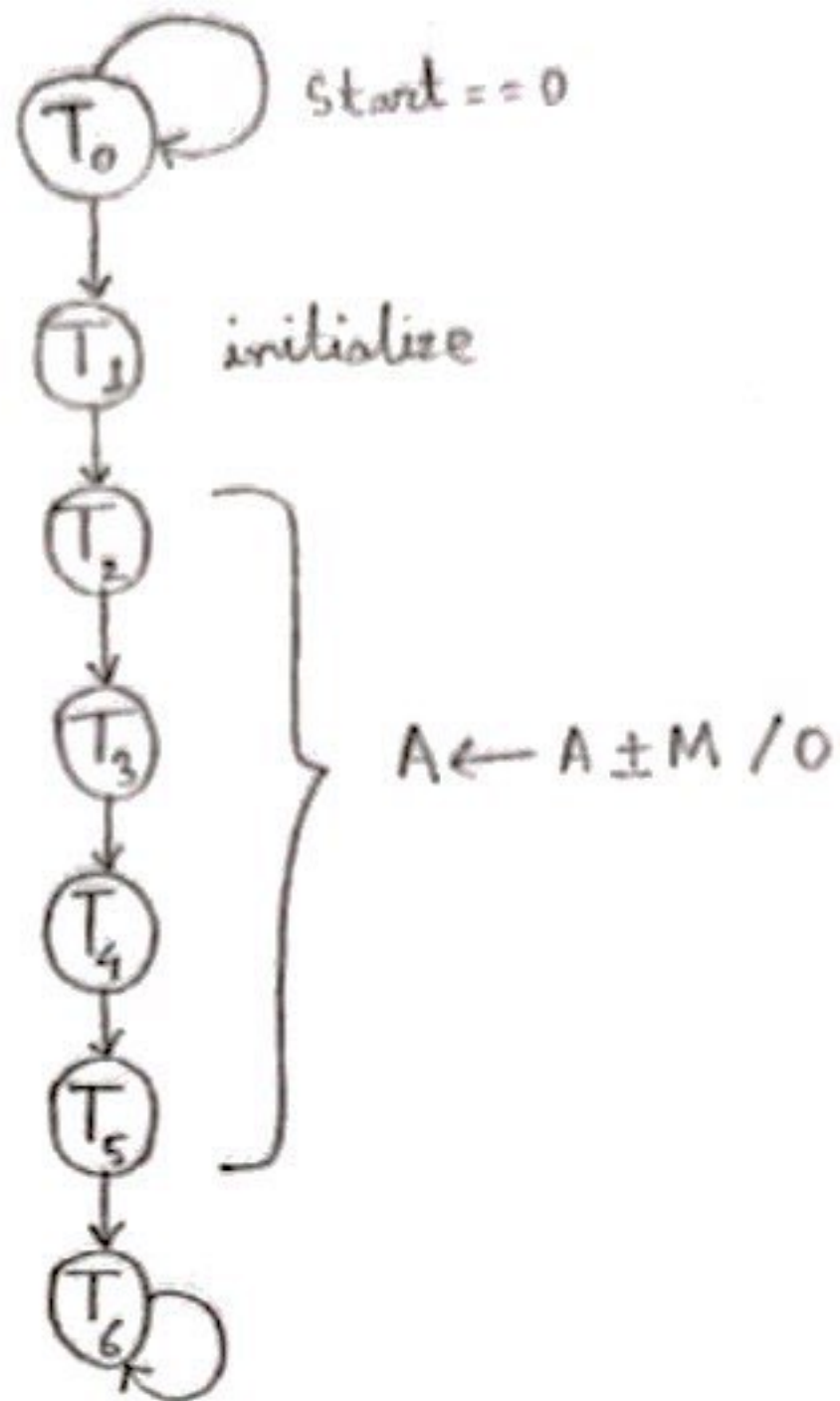

Control Signal:

State	$\overline{\text{Clear}}$	$\overline{\text{Load/Shift}}$	Clk-enable
T_0	0	0	1
T_1	1	0	1
T_2	1	1	1
T_3	1	1	1
T_4	1	1	1
T_5	1	1	1
T_6	1	1	0

Boolean Expression :

$$DT_0 = T_0 \overline{\text{Start}}$$

$$DT_1 = T_0 \text{Start}$$

$$DT_2 = T_1$$

$$DT_3 = T_2$$

$$DT_4 = T_3$$

$$DT_5 = T_4$$


$$DT_6 = T_5 + T_6$$


$$\overline{\text{Clear}} = T_1 + T_2 + T_3 + T_4 + T_5 + T_6$$

$$\overline{\text{Load/Shift}} = T_2 + T_3 + T_4 + T_5 + T_6$$

$$\text{Clk-enable} = T_0 + T_1 + T_2 + T_3 + T_4 + T_5$$

Control Unit Circuit :

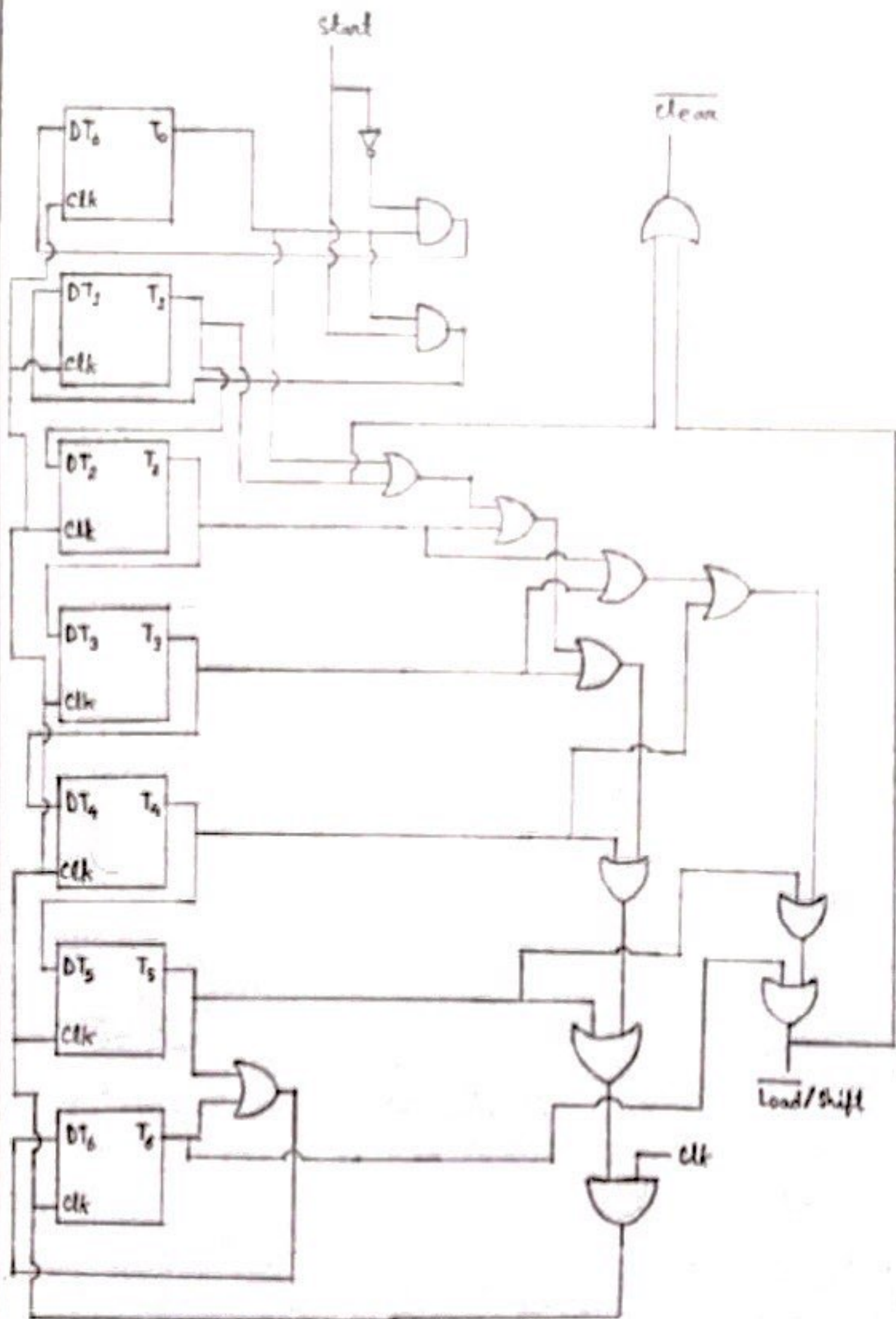

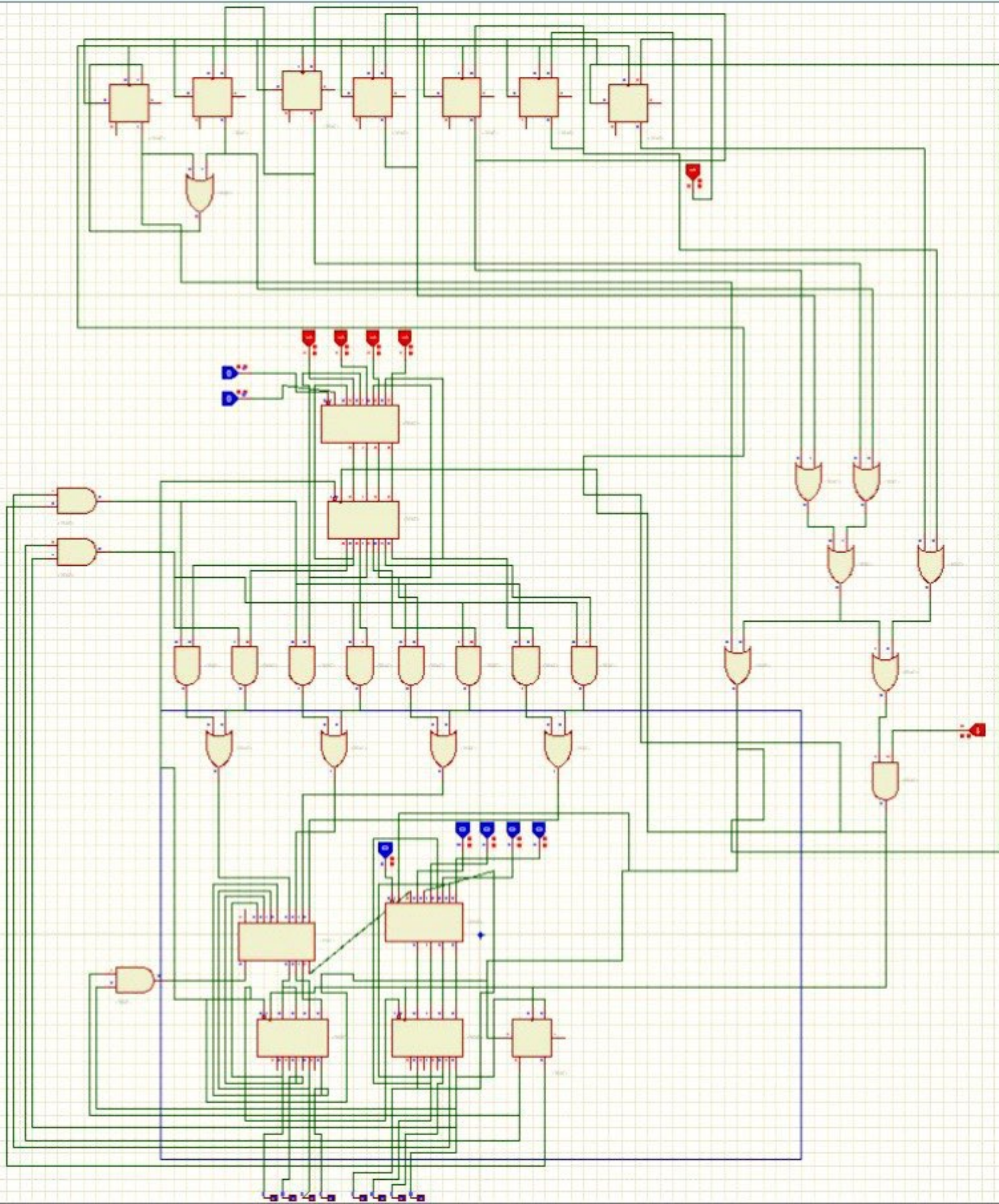

Conclusion:-

To design this circuit, we have used proteus simulating system and tested our multiplier with different values and got desired output. So, we can say that our circuit is working properly. During our work, we faced no error. Also, the total cost of performing the simulation was reasonable.